

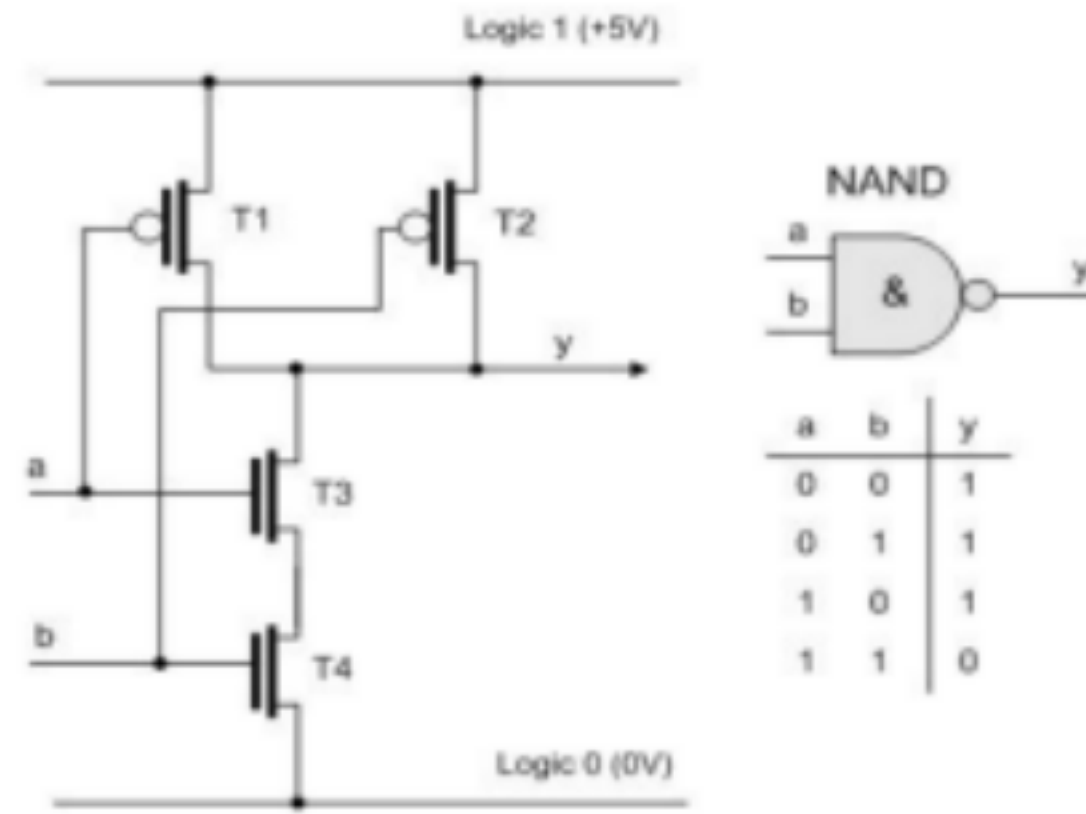


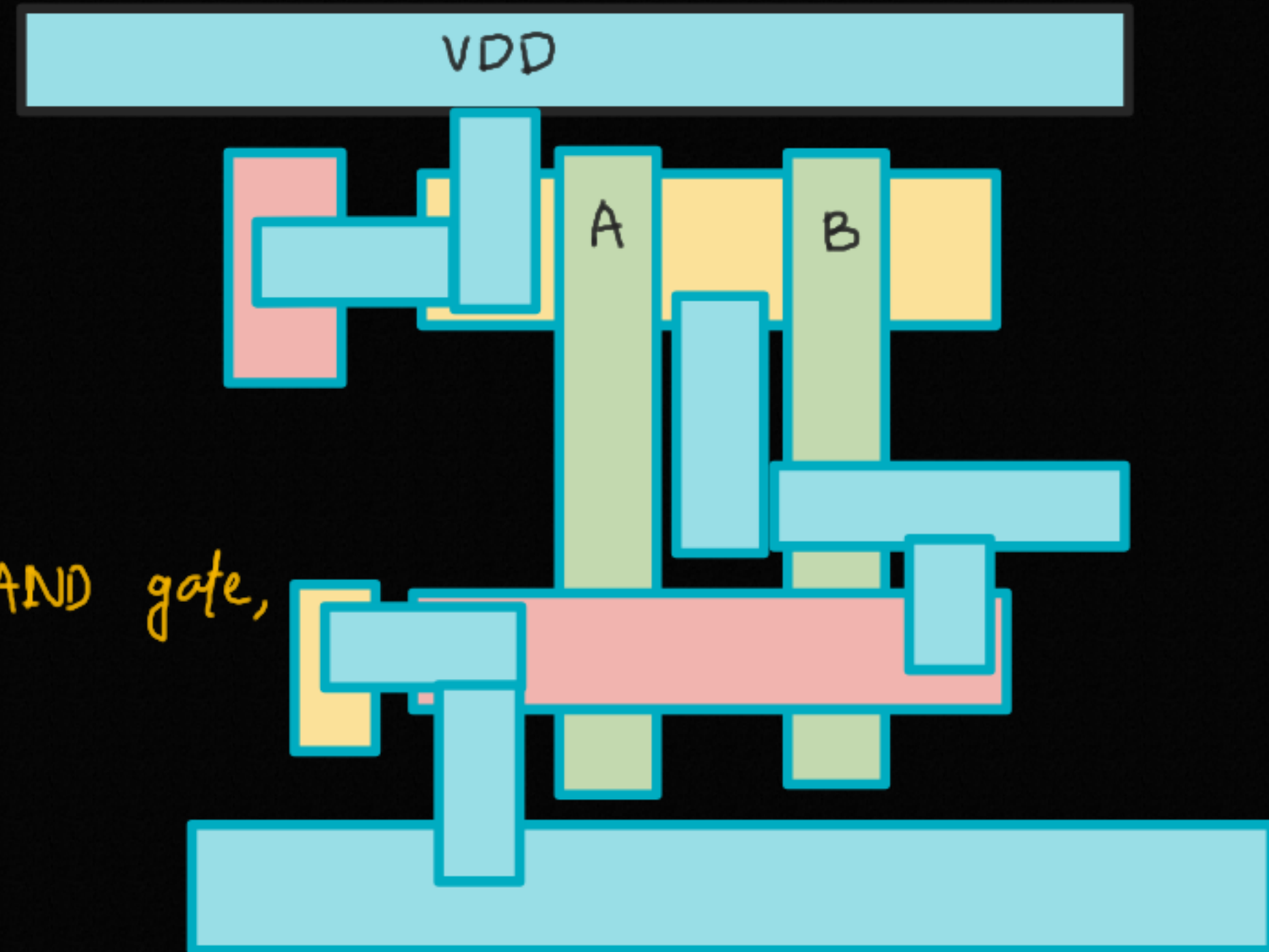Draw the Stick Diagram and the Layout for the NAND Gate Below



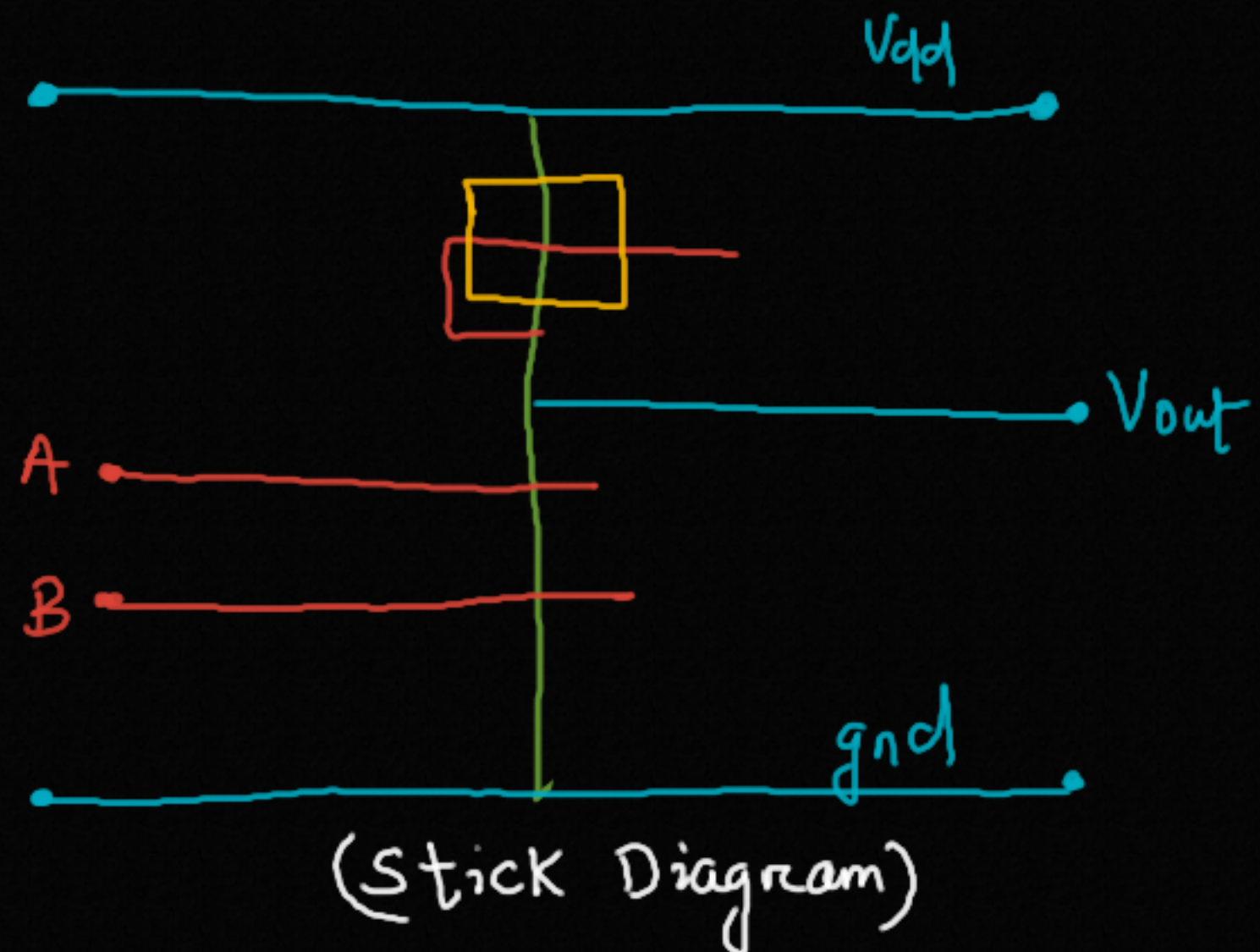Solution Stick diagram for 2-input NAND gate,





Draw the Stick Diagram and the Layout for the Complex Logic Gate Below

