

1. Explain the different modes of operation of a PNP transistor with required conditions and a suitable diagram. Draw the symbol of a PNP transistor with proper labeling.


Solution:-

PNP transistors have four different modes of operation:-

(a) Cut off region (b) Active region (c) Saturation region (d) Reverse active region

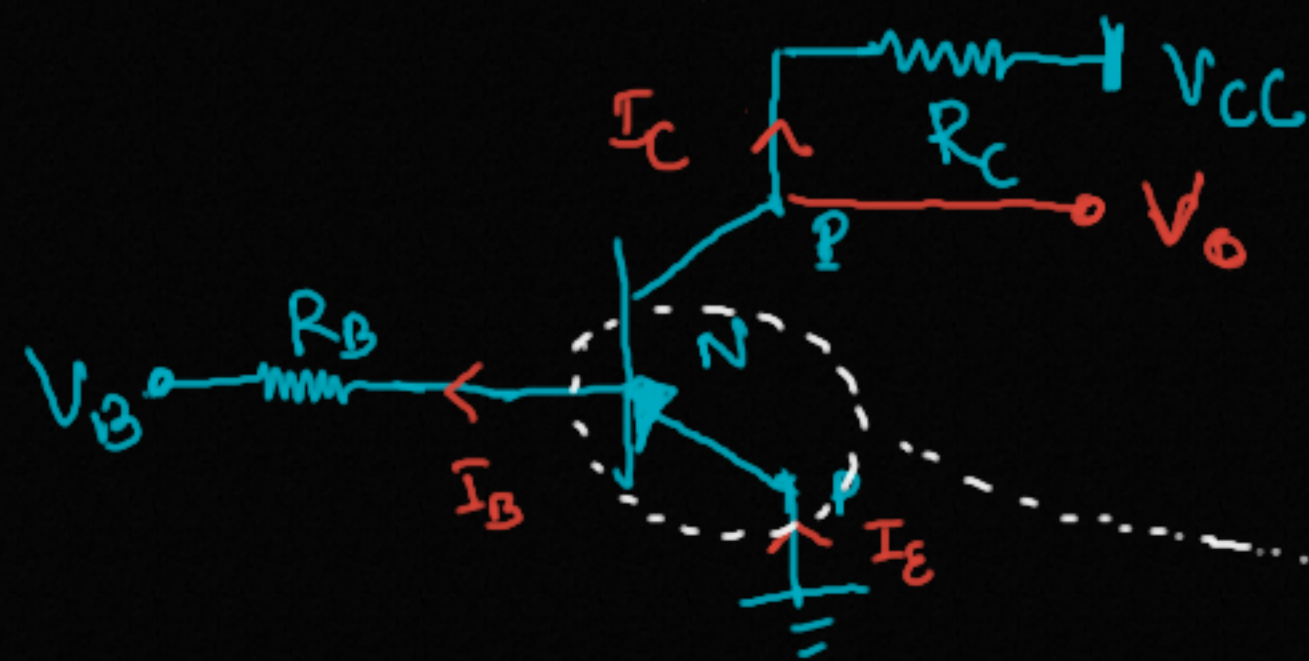(a) Cut off region:-

In this mode emitter base junction and collector base junction are reverse biased, where there is no flow of current in transistor. This mode can be used in switching operation where we need to switch off the circuit.



$$I_C = I_B = I_E = 0$$

$$V_O = V_{CC} - I_C R_C$$

$(V_{EB})_{o.c.}$ = open circuit voltage of
Emitter Base Junction


DC operating point

$$(V_{EB})_{o.c.} < 0.7V \text{ (for silicon transistor)}$$

$(0, V_{CC})$

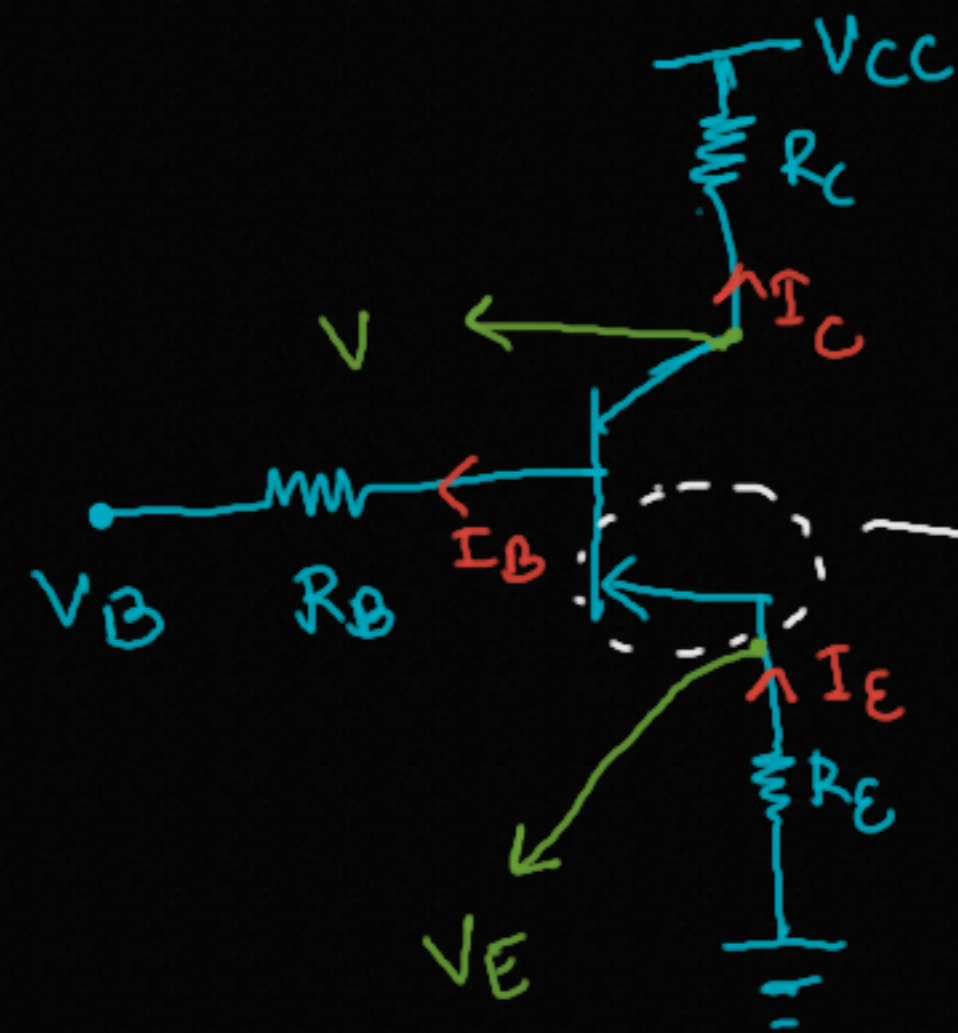(b) Active Region:-

In this mode of configuration, the emitter base junction is forward biased and collector base junction is reverse-biased. In this mode we use the transistor as an amplifier.



$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_C = \alpha I_E$$

$(V_{EB})_{O.C.} > 0.7V$
(for silicon transistor)


And also $(V_{CE}) > 0.2V$

V_{CE} = voltage
of collector emitter
junction

Dc operating Point
- $(I_C, V_{CC} - I_C R_C - V_E)$

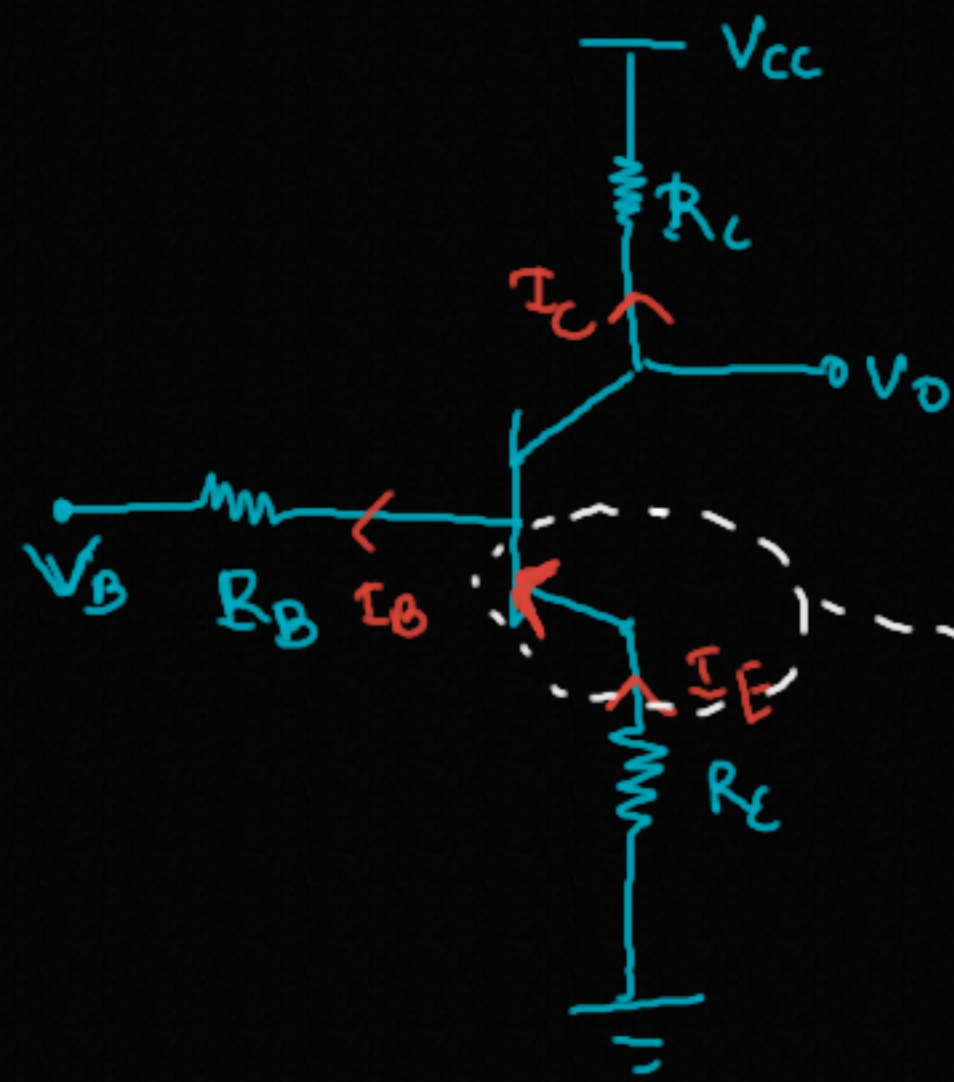(c) Saturation Region:-

In this mode of operation, both emitter base junction and collector base junction are forward biased. This can be used in switch application to turn on the switch.



$$I_C \neq \beta I_B$$

$$I_E = I_B + I_C$$


$$(V_{CE})_{sat} = 0.2V$$

(silicon transistor)

DC operating point
 $-(I_C, 0.2V)$

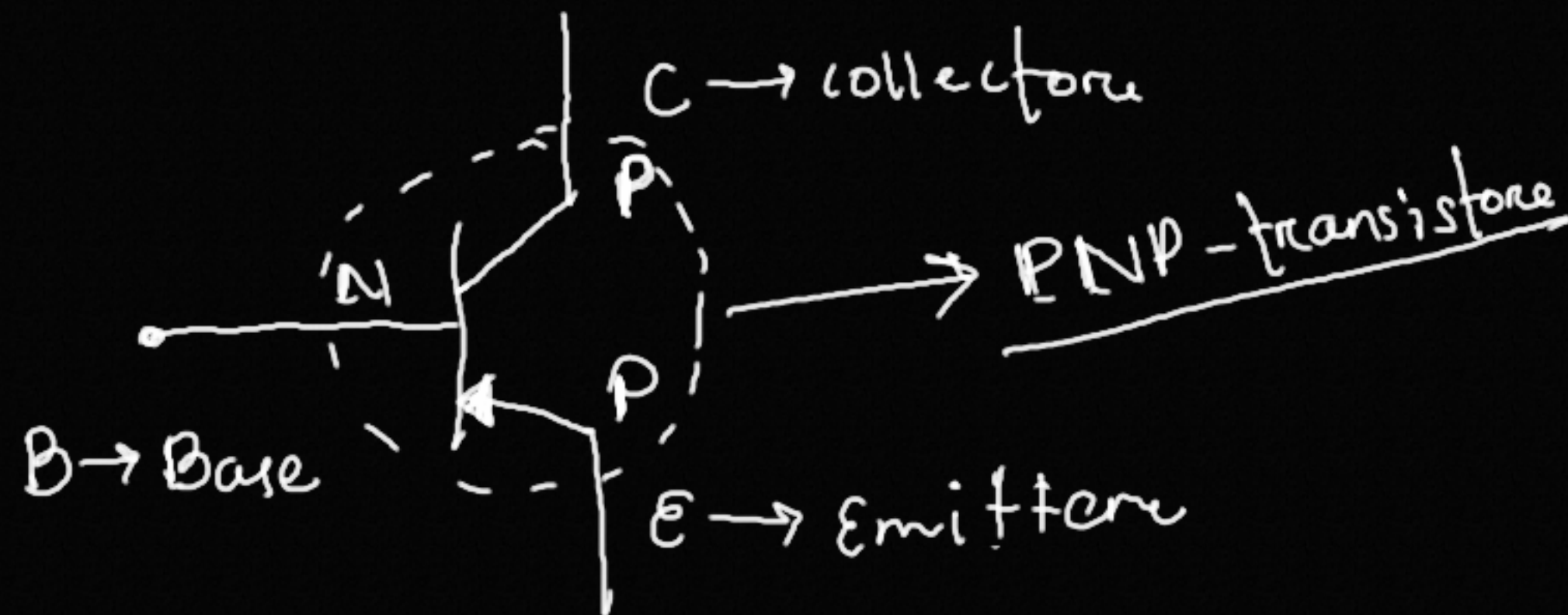
(d) Reverse Active:-

In this mode of operation, emitter base junction is forward biased whereas the collector base junction is reverse-biased. This mode is generally not used.



For the given circuit, if the voltage across $3.3\text{k}\Omega$ resistor is 5V , $V_{EB} = 0.7\text{V}$ and $\beta = 100$, then value of R_2 (in $\text{k}\Omega$) is —

Solution

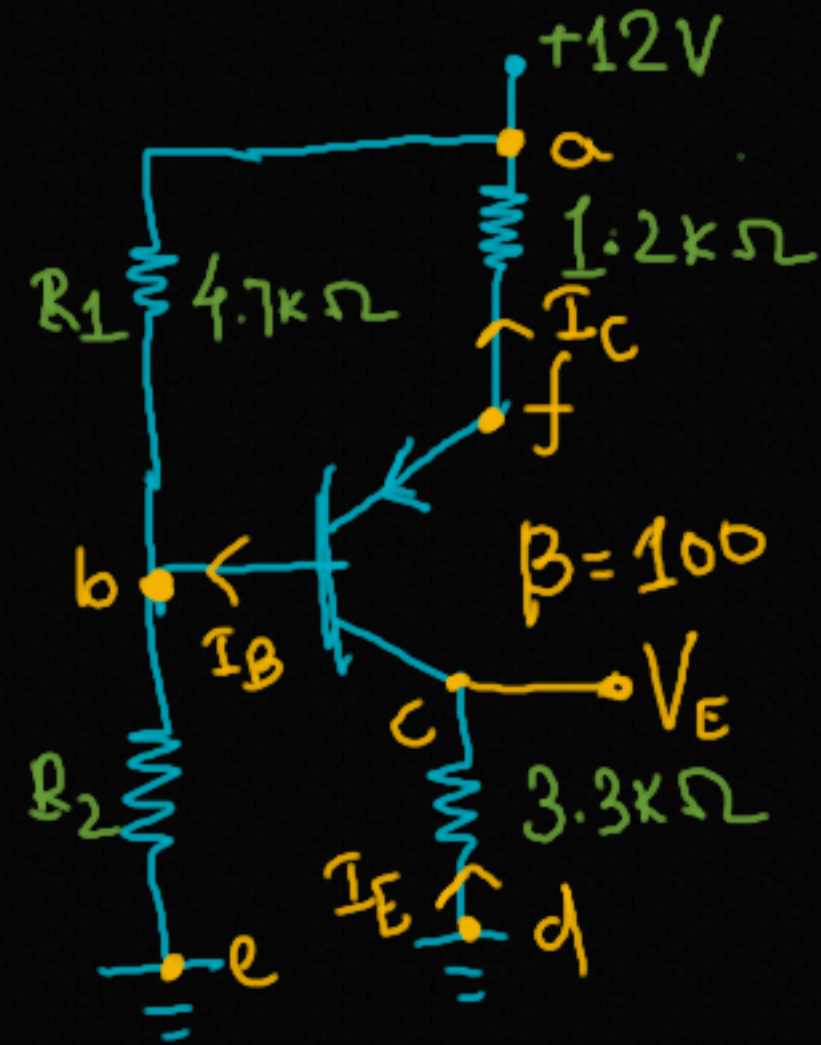

Given, In the transistor (PNP),

$$\beta = 100 \quad V_{CC} = 12\text{V} \quad V_E = 5\text{V} \quad V_{EB} = 0.7\text{V}$$

$$R_1 = 4.7\text{k}\Omega \quad R_C = 1.2\text{k}\Omega \quad R_E = 3.3\text{k}\Omega$$

Assume the transistor is in active region.

Then by applying in the loop afcd,


$$V_{CC} - I_C R_C - V_E - I_E R_E = 0$$

$$\Rightarrow V_{CC} - \beta I_B R_C - V_E - (\beta + 1) I_B R_E = 0 \quad (\because I_C = \beta I_B \text{ and } I_E = I_B + I_C)$$

$$\Rightarrow 12\text{V} - 100 I_B \times 1.2\text{k}\Omega - 5\text{V} - 101 I_B \times 3.3\text{k}\Omega = 0$$

$$\Rightarrow I_B = \frac{12\text{V} - 5\text{V}}{(100 \times 1.2 + 101 \times 3.3)\text{k}\Omega} = \frac{7\text{V}}{453.3\text{k}\Omega} = 0.015\text{mA}$$
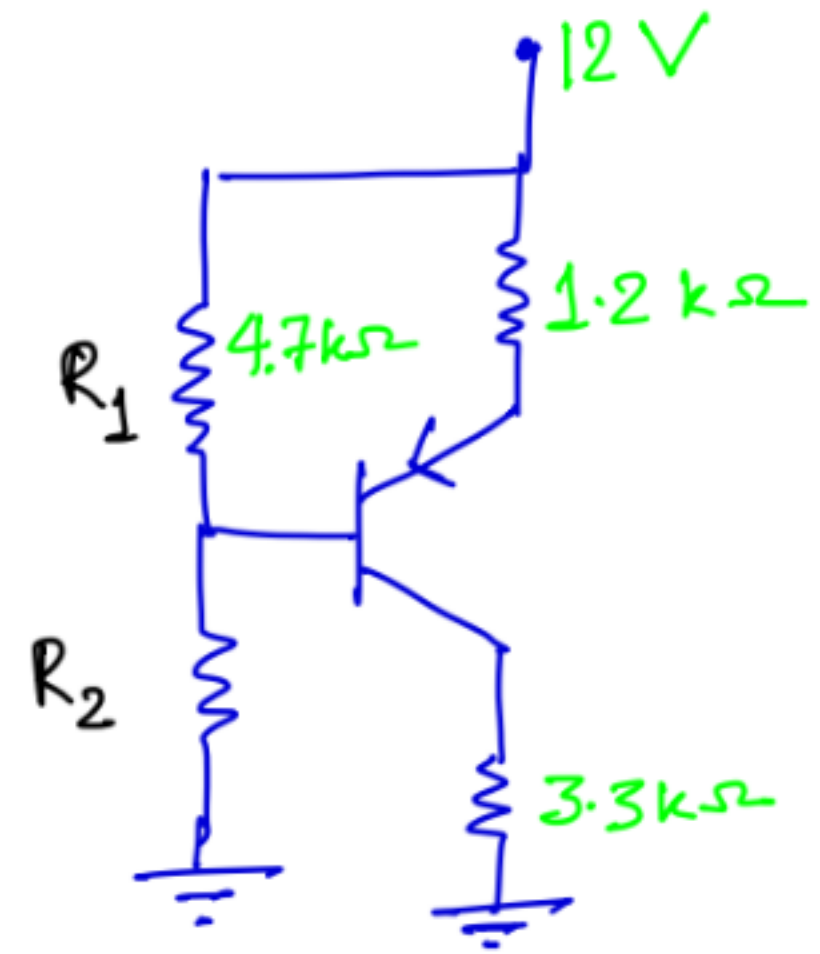
$$\text{Now, } I_C = \beta I_B = 100 \times 0.015\text{mA} = 1.5\text{mA} \text{ and } I_E = I_B + I_C = 1.515\text{mA}$$



Now, $I_C = 1.5 \text{ mA}$ $I_B = 0.015 \text{ mA}$ $I_E = 1.515 \text{ mA}$

Let I be the current flowing through $R_1 = 4.7 \text{ k}\Omega$.

Then by applying KVL in loop a b c d,

$$V_{CC} - I \times R_1 - V_{BE} - I_E R_E = 0$$

$$\Rightarrow 12 \text{ V} - I \times 4.7 \text{ k}\Omega + V_{EB} - I_E R_E = 0$$

$$\Rightarrow 12 \text{ V} - I \times 4.7 \text{ k}\Omega + 0.7 \text{ V} - 1.515 \text{ mA} \times 3.3 \text{ k}\Omega = 0$$

$$\Rightarrow 12 \text{ V} + 0.7 \text{ V} - 5 \text{ V} = I \times 4.7 \text{ k}\Omega \Rightarrow I = \frac{12.7 \text{ V} - 5 \text{ V}}{4.7 \text{ k}\Omega}$$

$$\Rightarrow I = \frac{7.7 \text{ V}}{4.7 \text{ k}\Omega} = 1.64 \text{ mA}$$

If the current flowing through the resistor is I_0 , then by applying KCL at node C,

$$I_0 = I_B + I = 0.015 \text{ mA} + 1.64 \text{ mA} = 1.655 \text{ mA}$$

If we apply KVL in loop abc,

$$V_{cc} - I_x R_1 - I_o R_2 = 0 \Rightarrow R_2 = \frac{V_{cc} - I_x R_1}{I_o}$$

$$\Rightarrow R_2 = \frac{12V - (1.64mA \times 4.7k\Omega)}{1.655mA} = \frac{12V - 7.71V}{1.655mA} = \frac{4.29V}{1.655mA} = 2.6k\Omega$$

∴ The resistance value will be (R_2) $2.6k\Omega$.

