

ASSIGNMENT-6

STA Assignment



Flop-1 and Flop-2 Data:


T_{setup}	62 ps
T_{hold}	10 ps
T_{pcq}	90 ps
T_{ccq}	75 ps

Combinational Circuit Data:

Component	T_{pd}	T_{cd}
Adder	590 ps	100 ps
Result MUX	60 ps	35 ps
Bypass MUX	80 ps	55 ps

If $T_{\text{clk}} = 815$ ps, then

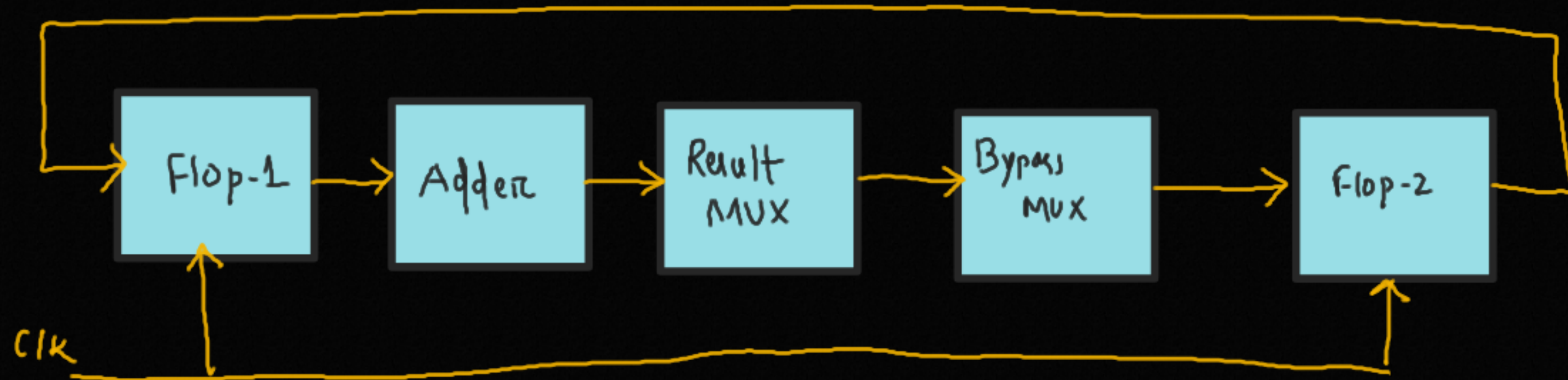- a) Is setup time violated?
- b) Is hold time violated?



$$T_{\text{setup}} = 62 \text{ ps}$$

$$T_{\text{hold}} = 10 \text{ ps}$$

$$T_{\text{prop}} = 90 \text{ ps}$$

$$T_{\text{cq}} = 75 \text{ ps}$$

$$\text{given, } T_{\text{clk}} = 815 \text{ ps}$$

$$T_{\text{pd}} = 590 \text{ ps}$$

$$T_{\text{cd}} = 100 \text{ ps}$$

$$T_{\text{pd}} = 60 \text{ ps}$$

$$T_{\text{cd}} = 35 \text{ ps}$$

$$T_{\text{pt}} = 80 \text{ ps}$$

$$T_{\text{cd}} = 55 \text{ ps}$$

$$T_{\text{setup}} = 62 \text{ ps}$$

$$T_{\text{hold}} = 10 \text{ ps}$$

$$T_{\text{pcq}} = 90 \text{ ps}$$

$$T_{\text{ccq}} = 75 \text{ ps}$$

In order to avoid set-up time violation, \therefore Hence, set-up time is violated.

$$T_{\text{clk}} \geq T_{\text{pd}} + T_{\text{pcq}} + T_{\text{set-up}}$$

$$T_{\text{pd}} + T_{\text{pcq}} + T_{\text{set-up}} = (590 + 60 + 80) + (90 + 90) + (62 + 62)$$

$$= 1034 \text{ ps}$$

$$\text{So, } T_{\text{clk}} \leq 1034 \text{ ps.}$$

(b) Hold Time:-

$$T_{hold} \leq T_{ccq} + T_{cd} \quad T_{hold} = 20 \text{ ps}$$

$$T_{ccq} + T_{cd} = (2 \times 75 \text{ ps}) + (100 + 35 + 55) \text{ ps}$$
$$= 340 \text{ ps}$$

$T_{hold} \leq 340 \text{ ps}$ \therefore Hence, the hold time is not violated.