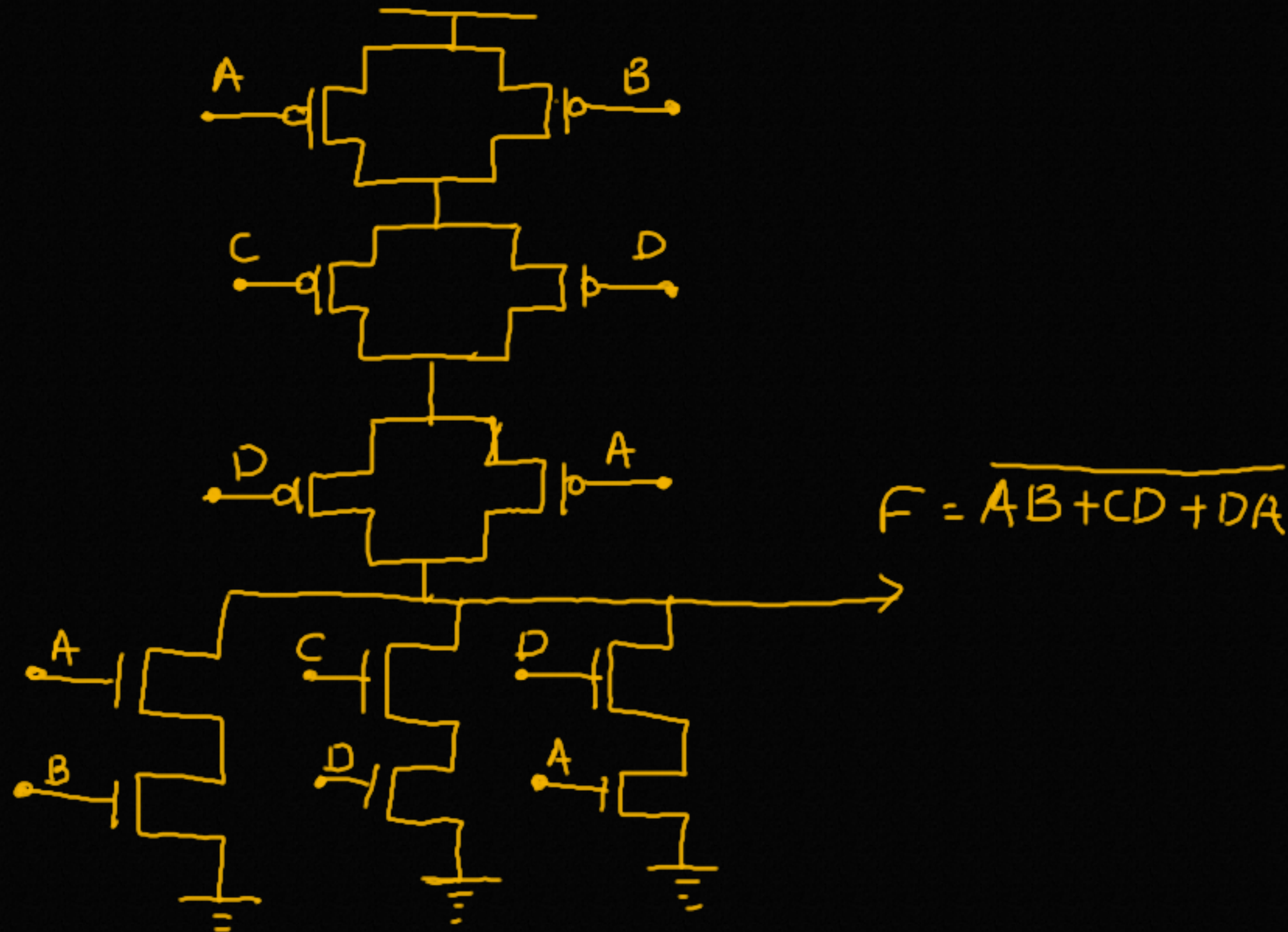



Assingment-5

Implement the Boolean function bar $(A.B + CD + DA)$ using CMOS logic family. Find the logical effort for each input. Approximate the delay using Elmore's delay method.

Solution


Boolean function $F = (AB + CD + DA)'$



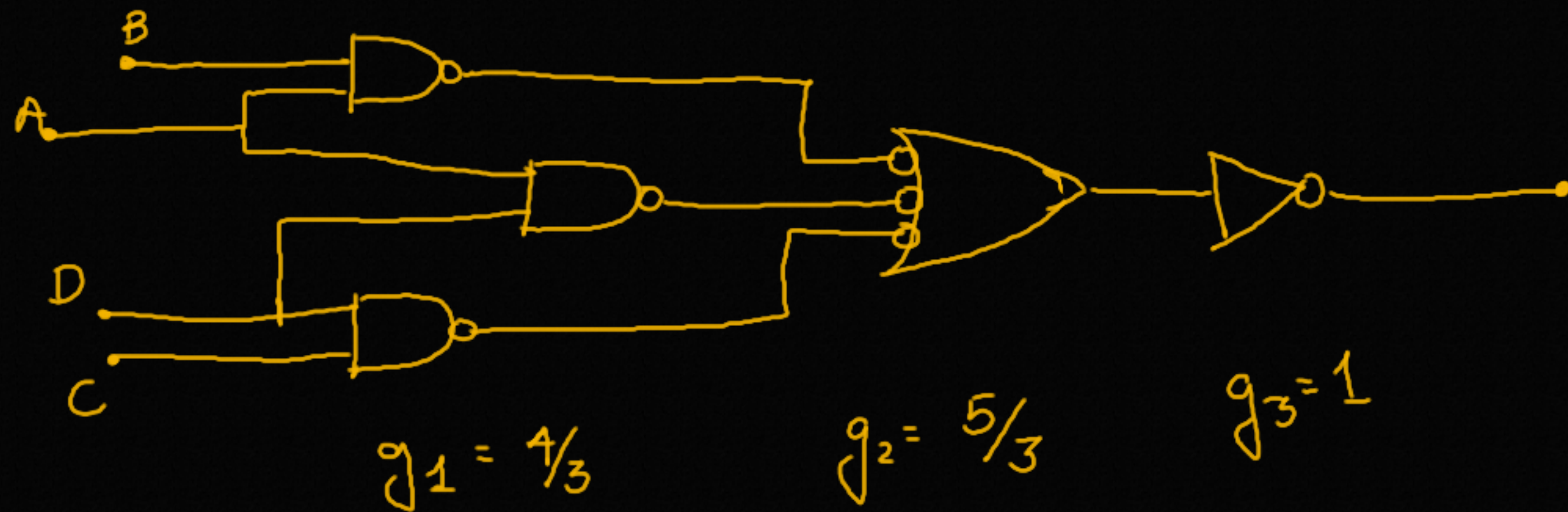

$$\text{logical effort} = \prod_{i=1}^3 g_i = \frac{4}{3} \times \frac{5}{3} \times 1 = \frac{20}{3}$$

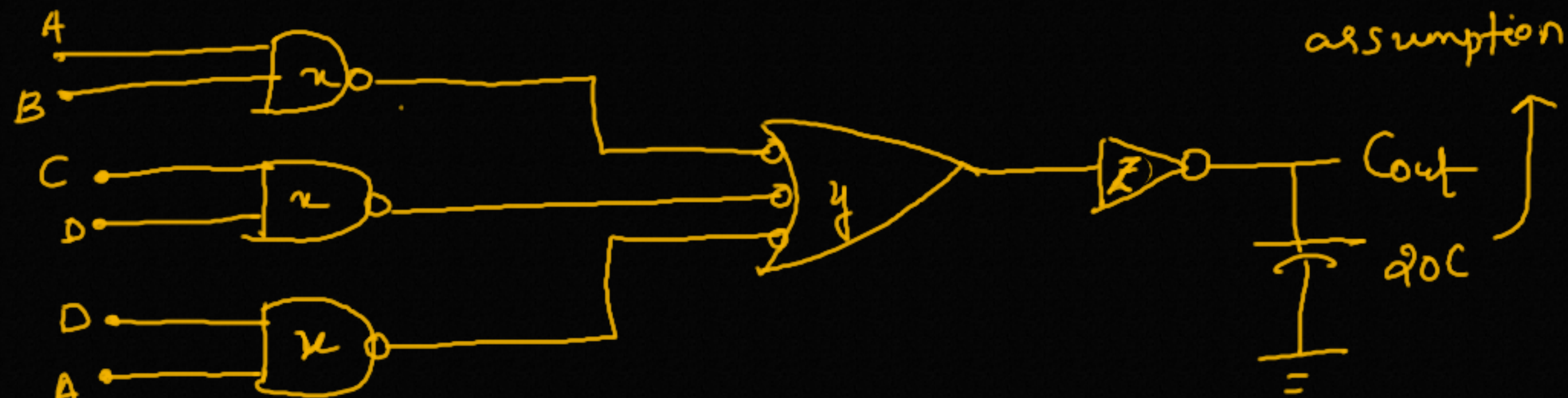\therefore logical effort for each input will be $\frac{20}{3}$.



Logical Effort

$$g_1 = \frac{4}{3}$$

$$p_1 = 2$$

$$h_1 = \frac{y}{x}$$

$$g_2 = \frac{5}{3}$$

$$p_2 = 3$$

$$h_2 = \frac{z}{y}$$

$$g_3 = 1$$

$$p_3 = 1$$

$$h_3 = \frac{20}{z}$$

as we know,

$$A.P. \leq G.P.$$

$$\Rightarrow (a+b+c+d) \leq (abcd)^{\frac{1}{4}}$$

$$\text{Delay} = p_1 + g_1 h_1 + p_2 + g_2 h_2 + p_3 + g_3 h_3$$

$$= 2 + \frac{4}{3} \cdot \frac{y}{x} + 3 + \frac{5}{3} \cdot \frac{z}{y} + 1 + \frac{20}{z} \times 1$$

$$= 6 + \frac{4}{3} \left(\frac{y}{x} \right) + \frac{5}{3} \cdot \frac{z}{y} + \frac{20}{z}$$

So, the maximum delay will be,

$$\text{delay} = 6 + \frac{4}{3} \times \frac{y}{x} \times \frac{5}{3} \times \frac{z}{y} \times \frac{20}{z} = 6 + \frac{400}{9x}$$

assume $x = 10$

$$\text{then delay} = 6 + \frac{40}{9}$$

$$= \frac{94}{9} = 10.44$$

\therefore The approximated delay will be 10.44.